4.3.1 Different electrical circuits

Look at the two circuits, shown in Figure 4.11. In Figure A two bulbs are connected in series and in Figure B they are connected in parallel. Let us look at each of these separately.

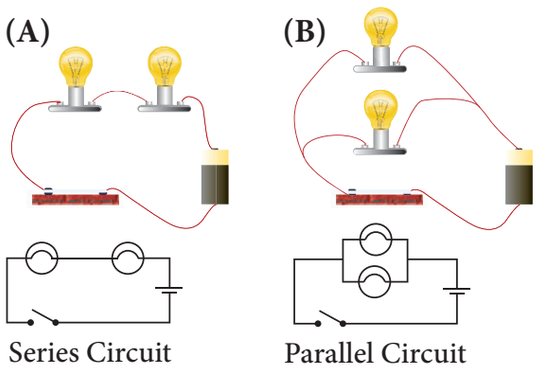


Figure 4.11 Series and parallel connections

Series circuits

Let us first look at the current in a series circuit. In a series circuit the components are connected one after another in a single loop. In a series circuit there is only one pathway through which the electric charge flow. From the above we can know that the current I all along the series circuit remain same. That is in a series circuit the current in each point of the circuit is same.

Parallel circuits


In parallel circuits, the components are connected to the e.m.f source in two or more loops. In a parallel circuit there is more than one path for the electric charge to flow. In a parallel circuit the sum of the individual current in each of the parallel branches is equal to the main current flowing into or out of the parallel branches. Also, in a parallel circuit the potential difference across separate parallel branches are same.

4.4 Effects of electric current

When current flows in a circuit it exhibits various effects. The main effects are heating, chemical and magnetic effects.

4.4.1 Heating effect

Activity 2

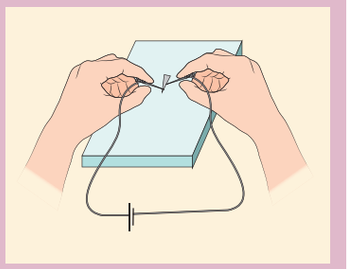

Cut an arrow shaped strip from aluminium foil. Ensure that the head is a fine point. Keep the arrow shaped foil on a wooden board. Connect a thin pin to two lengths of wire. Connect the wires to the terminals of electric cell, may be of 9V. Press one pin onto the pointed tip and other pin at a point about one or two mm away. Can you see that the tip of aluminium foil starts melting?



Caution: The heating effect and the chemical effect experiments have to be performed only with a dc cell of around 9V. Students at any cost **should not use** the main domestic electric supply which is a 220V ac voltage. If it is used it will give a heavy electric shock leading to a severe damage to our body.

When the flow of current is 'resisted' generally heat is produced. This is because the electrons while moving in the wire or resistor suffer resistance. Work has to be done to overcome the resistance which is converted in to heat energy. **This conversion of electrical energy into heating energy is called 'Joule heating'** as this effect was extensively studied by the scientist Joule. This forms the principle of all electric heating appliances like iron box, water heater, toaster etc. Even connecting wires offer a small resistance to the flow of current. That is why almost all electrical appliances including the connecting wires are warm when used in an electric circuit.

IX_SCI_EM_Unit-04_PHY.indd 45 12/7/2022 5:01:32 PM